

CDA 4213 001/CIS 6930 012
Fall 2017
CMOS VLSI Design

Lab 2 Report

Canvas Submission
Due: 11:59 PM, 1st Oct. 2017


Note: Upload PDF version of this report. Only PDF format is accepted.

Today's Date:	10/1/17
Your Name:	Alan Rodriguez
Your U Number:	86831061
No. of Hours Spent:	3
Exercise Difficulty: (Easy, Average, Hard)	Average
Any Other Feedback:	

Question 1 (5 pts): NMOS Transistor

Include the following

 - a) Transistor level diagram
- b) Spice netlist (.sp file contents)
- c) Waveform results
- d) Explain how you demonstrate that NMOS transistor is good (poor) conductor of 0 (1).




```
**-----
* NMOS SPICE deck
**-----
* Parameters and models
**-----
.include mosistsmc180.sp.txt
.options post list scale=1n

**-----
* Simulation netlist
**-----
Vdd Vdd 0 1.8V
Vin in 0 PULSE 0 1.8V 0.5ns 0.1ns 0.1ns 10ns 20ns

m1 out Vdd in 0 NMOS W=180 L=180

Cload out 0 0.01pF

 .tran 1ns 40ns
.plot V(in) V(out)
.end
```




By passing the VDD into the gate for the NMOS transistor, it is shown that the value is only "strong" for 0 and degrades for logic of 1.

 Question 2 (5 pts): PMOS Transistor

Include the following

- Transistor level diagram
- Spice netlist (.sp file contents)
- Waveform results
- Explain how you demonstrate that NMOS transistor is good (poor) conductor of 1 (0).



```
**-----
* PMOS SPICE deck
**-----
* Parameters and models
**-----
.include mosistsmc180.sp.txt
.options post list scale=1n

**-----
* Simulation netlist
**-----
Vdd Vdd 0 1.8V
Vin in 0 PULSE 0 1.8V 0.5ns 0.1ns 0.1ns 10ns 20ns

m1 out 0 in Vdd PMOS W=360 L=180

Cload out 0 0.01pF

.tran 1ns 40ns
.plot V(in) V(out)
.end
```




By passing the GND (0) into the gate for the PMOS transistor, it is shown that the value is only "strong" for 1 and degrades for logic of 0.

Question 3 (10 pts): Transmission Gate

Include the following

 - a) Transistor level diagram
- b) Spice netlist (.sp file contents)
- c) Waveform results




```
**-----
* Transmission Gate SPICE deck
**-----
* Parameters and models
**-----
.include mosistsmc180.sp.txt
.options post list scale=1n

**-----
* Simulation netlist
**-----
Vdd Vdd 0 1.8V
Vin in 0 PULSE 0 1.8V 0.5ns 0.1ns 0.1ns 4ns 8ns
Vin2 Clock 0 PULSE 0 1.8V 0.5ns 0.1ns 0.1ns 10ns 20ns
Vin3 Clockb 0 PULSE 1.8V 0 0.5ns 0.1ns 0.1ns 10ns 20ns

m1 out ClockB in Vdd PMOS W=360 L=180
m2 out Clock in 0 NMOS W=180 L=180
Cload out 0 0.01pF

 
.tran 1ns 40ns
.plot V(in) V(out)
.end
```



Question 4 (10 pts): 2-input Multiplexor

Include the following

 - a) Transistor level diagram
- b) Spice netlist (.sp file contents)
- c) Waveform results



```
**-----
* 2-input Multiplexer Gate SPICE deck
**-----
* Parameters and models
**-----
.include mosistsmc180.sp.txt
.options post list scale=1n

**-----
* Simulation netlist
**-----
Vdd Vdd 0 1.8V
Vd0 d0 0 PULSE 0 1.8V 0.5ns 0.1ns 0.1ns 4ns 8ns
vd1 d1 0 PULSE 1.8V 0 0.5ns 0.1ns 0.1ns 4ns 8ns
Vin in 0 PULSE 0 1.8V 0.5ns 0.1ns 0.1ns 4ns 8ns
Vin2 Clock 0 PULSE 0 1.8V 0.5ns 0.1ns 0.1ns 10ns 20ns
Vin3 Clockb 0 PULSE 1.8V 0 0.5ns 0.1ns 0.1ns 10ns 20ns

m1 out Clock d0 Vdd PMOS W=360 L=180
m2 out Clockb d0 0 NMOS W=180 L=180
m3 out Clockb d1 Vdd PMOS W=360 L=180
m4 out Clock d1 0 NMOS W=180 L=180

Cload out 0 0.01pF
.tran 1ns 40ns
.plot V(in) V(out)
.end
```